

## Coders Interface

*USBoxS manage 2 biphasic coders (HEDS-5701#A00 for example) but to adapt TTL signals to 2.5Vcc an internal resistors divider is wired (220/330Ω).*

*LECOEUR ELECTRONIQUE company suggest to add a Schmitt trigger (74AC14) between USBoxS and coders with an external power supply.*

